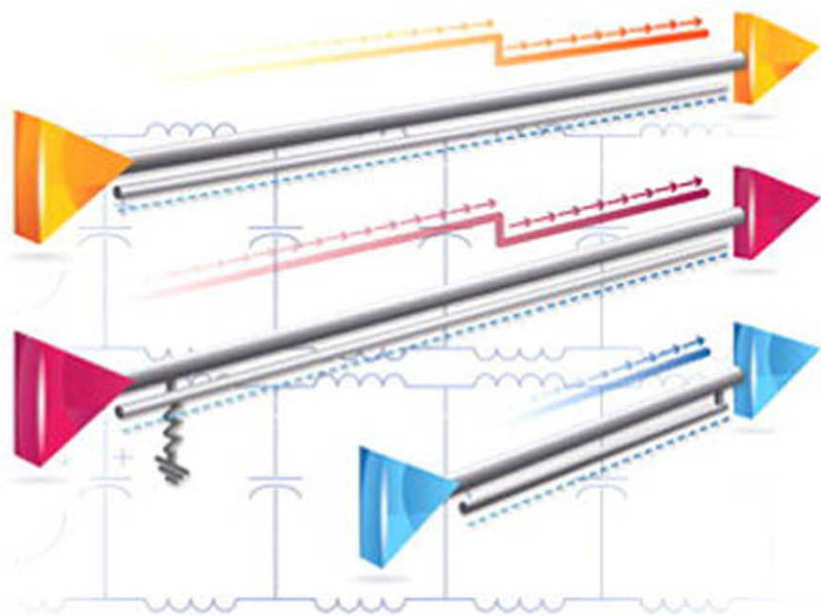


PCB Currents

How they Flow, How they React



Douglas Brooks

Modern Semiconductor Design Series
Signal Integrity Library

PCB Currents

PCB Currents: How They Flow, How They React

Table of Contents

Cover

Half Title

Title Page

Copyright Page

CONTENTS

PREFACE

Part I: NATURE OF CURRENT

1. Electrons and Charges
2. Basic Current Concepts
3. Basic Current Laws

Part II: CURRENT FLOW IN BASIC CIRCUITS

4. Resistive Circuits
5. Reactive Circuits: Capacitors and Capacitance
6. Reactive Circuits: Inductors and Inductance
7. Reactive Circuits: Resonance
8. Impedance
9. Real Components and Parasitics
10. Time Constants and Filters
11. Transformers

Table of Contents

12. Differential Current Flow

13. Semiconductors

Part III: VOLTAGE AND CURRENT SOURCES

14. Voltage and Current Sources

Part IV: CURRENT FLOW ON CIRCUIT BOARDS

15. Where Do Currents Flow on Circuit Boards

16. Current and Trace Temperatures

17. Current Reflections

18. Coupled Currents/EMI/Crosstalk

19. Current Distribution and Bypass Capacitors

20. Frequency-Variable Resistance and Lossy Transmission Lines

21. Currents and Vias

22. Current and Signal Integrity

Appendices

A: Current flow and Maxwell

B: Eye diagrams

C: Death of the Circuit Board

Index