

ELECTRONICS

A SYSTEMS APPROACH

SIXTH EDITION



Pearson

NEIL STOREY

ELECTRONICS

A SYSTEMS APPROACH

Electronics

Table of Contents

Cover

Title Page

Copyright Page

Brief Contents

Contents

Preface

List of Videos

Acknowledgements

Publishers Acknowledgements

Part 1 ELECTRICAL CIRCUITS AND COMPONENTS

1 Basic Electrical Circuits and Components

1.1 Introduction

1.2 Système International units

1.3 Common prefixes

1.4 Electrical circuits

1.5 Direct current and alternating current

1.6 Resistors, capacitors and inductors

1.7 Ohms law

1.8 Kirchhoffs laws

1.9 Power dissipation in resistors

1.10 Resistors in series

1.11 Resistors in parallel

1.12 Resistive potential dividers

1.13 Sinusoidal quantities

1.14 Circuit symbols

Table of Contents

Further study

Key points

Exercises

2 Measurement of Voltages and Currents

2.1 Introduction

2.2 Sine waves

2.3 Square waves

2.4 Measuring voltages and currents

2.5 Analogue ammeters and voltmeters

2.6 Digital multimeters

2.7 Oscilloscopes

Further study

Key points

Exercises

3 Resistance and DC Circuits

3.1 Introduction

3.2 Current and charge

3.3 Voltage sources

3.4 Current sources

3.5 Resistance and Ohms law

3.6 Resistors in series and parallel

3.7 Kirchhoffs laws

3.8 Thévenins theorem and Nortons theorem

3.9 Superposition

3.10 Nodal analysis

3.11 Mesh analysis

3.12 Solving simultaneous circuit equations

3.13 Choice of techniques

Further study

Key points

Exercises

4 Capacitance and Electric Fields

Table of Contents

- 4.1 Introduction
- 4.2 Capacitors and capacitance
- 4.3 Capacitors and alternating voltages and currents
- 4.4 The effect of a capacitors dimensions on its capacitance
- 4.5 Electric field strength and electric flux density
- 4.6 Capacitors in series and in parallel
- 4.7 Relationship between voltage and current in a capacitor
- 4.8 Sinusoidal voltages and currents
- 4.9 Energy stored in a charged capacitor
- 4.10 Circuit symbols
- Further study
- Key points
- Exercises

5 Inductance and Magnetic Fields

- 5.1 Introduction
- 5.2 Electromagnetism
- 5.3 Reluctance
- 5.4 Inductance
- 5.5 Self-inductance
- 5.6 Inductors
- 5.7 Inductors in series and in parallel
- 5.8 Relationship between voltage and current in an inductor
- 5.9 Sinusoidal voltages and currents
- 5.10 Energy storage in an inductor
- 5.11 Mutual inductance
- 5.12 Transformers
- 5.13 Circuit symbols
- 5.14 The use of inductance in sensors
- Further study
- Key points
- Exercises

6 Alternating Voltages and Currents

Table of Contents

- 6.1 Introduction
- 6.2 Relationship between voltage and current
- 6.3 Reactance of inductors and capacitors
- 6.4 Phasor diagrams
- 6.5 Impedance
- 6.6 Complex notation
- Further study
- Key points
- Exercises

7 Power in AC Circuits

- 7.1 Introduction
- 7.2 Power dissipation in resistive components
- 7.3 Power in capacitors
- 7.4 Power in inductors
- 7.5 Power in circuits with resistance and reactance
- 7.6 Active and reactive power
- 7.7 Power factor correction
- 7.8 Three-phase systems
- 7.9 Power measurement
- Further study
- Key points
- Exercises

8 Frequency Characteristics of AC Circuits

- 8.1 Introduction
- 8.2 Two-port networks
- 8.3 The decibel (dB)
- 8.4 Frequency response
- 8.5 A high-pass RC network
- 8.6 A low-pass RC network
- 8.7 A low-pass RL network
- 8.8 A high-pass RL network
- 8.9 A comparison of RC and RL networks

Table of Contents

- 8.10 Bode diagrams
- 8.11 Combining the effects of several stages
- 8.12 RLC circuits and resonance
- 8.13 Filters
- 8.14 Stray capacitance and inductance
- Further study
- Key points
- Exercises

9 Transient Behaviour

- 9.1 Introduction
- 9.2 Charging of capacitors and energizing of inductors
- 9.3 Discharging of capacitors and de-energising of inductors
- 9.4 Generalised response of first-order systems
- 9.5 Second-order systems
- 9.6 Higher-order systems
- Further study
- Key points
- Exercises

10 Electric Motors and Generators

- 10.1 Introduction
- 10.2 A simple AC generator
- 10.3 A simple DC generator
- 10.4 DC generators or dynamos
- 10.5 AC generators or alternators
- 10.6 DC motors
- 10.7 AC motors
- 10.8 Universal motors
- 10.9 Stepper motors
- 10.10 Electrical machines a summary
- Further study
- Key points
- Exercises

Table of Contents

Part 2 ELECTRONIC SYSTEMS

11 Electronic Systems

- 11.1 Introduction
- 11.2 A systems approach to engineering
- 11.3 Systems
- 11.4 System inputs and outputs
- 11.5 Physical quantities and electrical signals
- 11.6 System block diagrams
- Further study
- Key points
- Exercises

12 Sensors

- 12.1 Introduction
- 12.2 Describing sensor performance
- 12.3 Temperature sensors
- 12.4 Light sensors
- 12.5 Force sensors
- 12.6 Displacement sensors
- 12.7 Motion sensors
- 12.8 Sound sensors
- 12.9 Sensor interfacing
- 12.10 Sensors a summary
- Further study
- Key points
- Exercises

13 Actuators

- 13.1 Introduction
- 13.2 Heat actuators
- 13.3 Light actuators
- 13.4 Force, displacement and motion actuators
- 13.5 Sound actuators

Table of Contents

13.6 Actuator interfacing

13.7 Actuators a summary

Further study

Key points

Exercises

14 Amplification

14.1 Introduction

14.2 Electronic amplifiers

14.3 Sources and loads

14.4 Equivalent circuit of an amplifier

14.5 Output power

14.6 Power gain

14.7 Frequency response and bandwidth

14.8 Differential amplifiers

14.9 Simple amplifiers

Further study

Key points

Exercises

15 Control and Feedback

15.1 Introduction

15.2 Open-loop and closed-loop systems

15.3 Automatic control systems

15.4 Feedback systems

15.5 Negative feedback

15.6 The effects of negative feedback

15.7 Negative feedback a summary

Further study

Key points

Exercises

16 Operational Amplifiers

16.1 Introduction

16.2 An ideal operational amplifier

Table of Contents

- 16.3 Some basic operational amplifier circuits
- 16.4 Some other useful circuits
- 16.5 Real operational amplifiers
- 16.6 Selecting component values for op-amp circuits
- 16.7 The effects of feedback on op-amp circuits
- Further study
- Key points
- Exercises

17 Semiconductors and Diodes

- 17.1 Introduction
- 17.2 Electrical properties of solids
- 17.3 Semiconductors
- 17.4 pn junctions
- 17.5 Diodes
- 17.6 Semiconductor diodes
- 17.7 Special-purpose diodes
- 17.8 Diode circuits
- Further study
- Key points
- Exercises

18 Field-effect Transistors

- 18.1 Introduction
- 18.2 An overview of field-effect transistors
- 18.3 Insulated-gate field-effect transistors
- 18.4 Junction-gate field-effect transistors
- 18.5 FET characteristics
- 18.6 FET amplifiers
- 18.7 Other FET applications
- 18.8 FET circuit examples
- Further study
- Key points
- Exercises

Table of Contents

19 Bipolar Junction Transistors

- 19.1 Introduction
- 19.2 An overview of bipolar transistors
- 19.3 Bipolar transistor operation
- 19.4 A simple amplifier
- 19.5 Bipolar transistor characteristics
- 19.6 Bipolar amplifier circuits
- 19.7 Bipolar transistor applications
- 19.8 Circuit examples
- Further study
- Key points
- Exercises

20 Power Electronics

- 20.1 Introduction
- 20.2 Bipolar transistor power amplifiers
- 20.3 Classes of amplifier
- 20.4 Power amplifiers
- 20.5 Four-layer devices
- 20.6 Power supplies and voltage regulators
- Further study
- Key points
- Exercises

21 Internal Circuitry of Operational Amplifiers

- 21.1 Introduction
- 21.2 Bipolar operational amplifiers
- 21.3 CMOS operational amplifiers
- 21.4 BiFET operational amplifiers
- 21.5 BiMOS operational amplifiers
- Further study
- Key points
- Exercises

22 Noise and Electromagnetic Compatibility

Table of Contents

- 22.1 Introduction
- 22.2 Noise sources
- 22.3 Representing noise sources within equivalent circuits
- 22.4 Noise in bipolar transistors
- 22.5 Noise in FETs
- 22.6 Signal-to-noise ratio
- 22.7 Noise figure
- 22.8 Designing for low-noise applications
- 22.9 Electromagnetic compatibility
- 22.10 Designing for EMC
- Further study
- Key points
- Exercises

23 Positive Feedback, Oscillators and Stability

- 23.1 Introduction
- 23.2 Oscillators
- 23.3 Stability
- Further study
- Key points
- Exercises

24 Digital Systems

- 24.1 Introduction
- 24.2 Binary quantities and variables
- 24.3 Logic gates
- 24.4 Boolean algebra
- 24.5 Combinational logic
- 24.6 Boolean algebraic manipulation
- 24.7 Algebraic simplification
- 24.8 Karnaugh maps
- 24.9 Automated methods of minimisation
- 24.10 Propagation delay and hazards
- 24.11 Number systems and binary arithmetic

Table of Contents

24.12 Numeric and alphabetic codes

24.13 Examples of combinational logic design

Further study

Key points

Exercises

25 Sequential Logic

25.1 Introduction

25.2 Bistables

25.3 Monostables or one-shots

25.4 Astables

25.5 Timers

25.6 Memory registers

25.7 Shift registers

25.8 Counters

25.9 Design of sequential logic circuits

Further study

Key points

Exercises

26 Digital Devices

26.1 Introduction

26.2 Gate characteristics

26.3 Logic families

26.4 TTL

26.5 CMOS

26.6 Interfacing TTL and CMOS or logic using different supply voltages

26.7 Power dissipation in digital systems

26.8 Noise and EMC in digital systems

Further study

Key points

Exercises

27 Implementing Digital Systems

27.1 Introduction

Table of Contents

27.2 Array logic

27.3 Microprocessors

27.4 System-on-a-chip (SOC) devices

27.5 Programmable logic controllers (PLCs)

27.6 Single-board computers and microcontrollers

27.7 Selecting an implementation method

Further study

Key points

Exercises

28 Data Acquisition and Conversion

28.1 Introduction

28.2 Sampling

28.3 Signal reconstruction

28.4 Data converters

28.5 Sample and hold gates

28.6 Multiplexing

Further study

Key points

Exercises

29 Communications

29.1 Introduction

29.2 The communications channel

29.3 Modulation

29.4 Demodulation

29.5 Multiplexing

29.6 Radio receivers

29.7 Microwave communication

29.8 Fibre-optic communication

Further study

Key points

Exercises

30 System Design

Table of Contents

30.1 Introduction

30.2 Design methodology

30.3 Choice of technology

30.4 Electronic design tools

Further study

Key points

Exercises

Appendices A Symbols

B SI units and prefixes

C Op-amp circuits

D Complex numbers

E Answers to selected exercises

Index