

GLOBAL
EDITION



Electronic Devices

Conventional Current Version

TENTH EDITION

Thomas L. Floyd



Pearson

ELECTRONIC DEVICES

Conventional Current Version

Tenth Edition

Global Edition

Electronic Devices, Global Edition

Table of Contents

Cover

Title Page

Copyright Page

Preface

Acknowledgments

Brief Contents

Contents

1. Introduction to Semiconductors

- 11. The Atom
- 12. Materials Used in Electronic Devices
- 13. Current in Semiconductors
- 14. N-Type and P-Type Semiconductors
- 15. The PN Junction

2. Diodes and Applications

- 21. Diode Operation
- 22. Voltage-Current Characteristic of a Diode
- 23. Diode Approximations
- 24. Half-Wave Rectifiers
- 25. Full-Wave Rectifiers
- 26. Power Supply Filters and Regulators
- 27. Diode Limiters and Clampers
- 28. Voltage Multipliers
- 29. The Diode Datasheet
- 210. Troubleshooting
- Device Application

3. Special-Purpose Diodes

- 31. The Zener Diode
- 32. Zener Diode Applications

Table of Contents

- 33. Varactor Diodes
- 34. Optical Diodes
- 35. The Solar Cell
- 36. Other Types of Diodes
- 37. Troubleshooting
- Device Application

4. Bipolar Junction Transistors

- 41. Bipolar Junction Transistor (BJT) Structure
- 42. Basic BJT Operation
- 43. BJT Characteristics and Parameters
- 44. The BJT as an Amplifier
- 45. The BJT as a Switch
- 46. The Phototransistor
- 47. Transistor Categories and Packaging
- 48. Troubleshooting
- Device Application

5. Transistor Bias Circuits

- 51. The DC Operating Point
- 52. Voltage-Divider Bias
- 53. Other Bias Methods
- 54. Troubleshooting
- Device Application

6. BJT Amplifiers

- 61. Amplifier Operation
- 62. Transistor AC Models
- 63. The Common-Emitter Amplifier
- 64. The Common-Collector Amplifier
- 65. The Common-Base Amplifier
- 66. Multistage Amplifiers
- 67. The Differential Amplifier
- 68. Troubleshooting
- Device Application

7. BJT Power Amplifiers

Table of Contents

- 71. The Class A Power Amplifier
- 72. The Class B and Class AB Push-Pull Amplifiers
- 73. The Class C Amplifier
- 74. Troubleshooting
- Device Application
- 8. Field-Effect Transistors (FETs)
 - 81. The JFET
 - 82. JFET Characteristics and Parameters
 - 83. JFET Biasing
 - 84. The Ohmic Region
 - 85. The MOSFET
 - 86. MOSFET Characteristics and Parameters
 - 87. MOSFET Biasing
 - 88. The IGBT
 - 89. Troubleshooting
 - Device Application
- 9. FET Amplifiers and Switching Circuits
 - 91. The Common-Source Amplifier
 - 92. The Common-Drain Amplifier
 - 93. The Common-Gate Amplifier
 - 94. The Class D Amplifier
 - 95. MOSFET Analog Switching
 - 96. MOSFET Digital Switching
 - 97. Troubleshooting
 - Device Application
- 10. Amplifier Frequency Response
 - 101. Basic Concepts
 - 102. The Decibel
 - 103. Low Frequency Amplifier Response
 - 104. High-Frequency Amplifier Response
 - 105. Total Amplifier Frequency Response
 - 106. Frequency Response of Multistage Amplifiers
 - 107. Frequency Response Measurements

Table of Contents

Device Application

11. Thyristors

111. The Four-Layer Diode

112. The Silicon-Controlled Rectifier (SCR)

113. SCR Applications

114. The Diac and Triac

115. The Silicon-Controlled Switch (SCS)

116. The Unijunction Transistor (UJT)

117. The Programmable Unijunction Transistor (PUT)

Device Application

12. The Operational Amplifier

121. Introduction to Operational Amplifiers

122. Op-Amp Input Modes and Parameters

123. Negative Feedback

124. Op-Amps with Negative Feedback

125. Effects of Negative Feedback on Op-Impedances

126. Bias Current and Offset Voltage

127. Open-Loop Frequency and Phase Responses

128. Closed-Loop Frequency Response

129. Troubleshooting

Device Application

Programmable Analog Technology

13. Basic Op-Amp Circuits

131. Comparators

132. Summing Amplifiers

133. Integrators and Differentiators

134. Troubleshooting

Device Application

Programmable Analog Technology

14. Special-Purpose Integrated Circuits

141. Instrumentation Amplifiers

142. Isolation Amplifiers

143. Operational Transconductance Amplifiers (OTAs)

Table of Contents

- 144. Log and Antilog Amplifiers
- 145. Converters and Other Integrated Circuits
- Device Application
- Programmable Analog Technology

15. Active Filters

- 151. Basic Filter Responses
- 152. Filter Response Characteristics
- 153. Active Low-Pass Filters
- 154. Active High-Pass Filters
- 155. Active Band-Pass Filters
- 156. Active Band-Stop Filters
- 157. Filter Response Measurements
- Device Application
- Programmable Analog Technology

16. Oscillators

- 161. The Oscillator
- 162. Feedback Oscillators
- 163. Oscillators with RC Feedback Circuits
- 164. Oscillators with LC Feedback Circuits
- 165. Relaxation Oscillators
- 166. The 555 Timer as an Oscillator
- Device Application
- Programmable Analog Technology

17. Voltage Regulators

- 171. Voltage Regulation
- 172. Basic Linear Series Regulators
- 173. Basic Linear Shunt Regulators
- 174. Basic Switching Regulators
- 175. Integrated Circuit Voltage Regulators
- 176. Integrated Circuit Voltage Regulator Configurations
- Device Application

Answers to Odd-Numbered Problems

Glossary

Table of Contents

Index