

GLOBAL  
EDITION



# Digital Design

*With an Introduction to the Verilog  
HDL, VHDL, and SystemVerilog*

SIXTH EDITION

M. Morris Mano • Michael D. Ciletti



Pearson

# Digital Design

---

With an Introduction to the Verilog HDL,  
VHDL, and SystemVerilog

# Digital Design, Global Edition

## Table of Contents

Front Cover

Tilte Page

Copyright Page

Contents

Preface

### 1 Digital Systems and Binary Numbers

1.1 Digital Systems

1.2 Binary Numbers

1.3 NumberBase Conversions

1.4 Octal and Hexadecimal Numbers

1.5 Complements of Numbers

1.6 Signed Binary Numbers

1.7 Binary Codes

1.8 Binary Storage and Registers

1.9 Binary Logic

### 2 Boolean Algebra and Logic Gates

2.1 Introduction

2.2 Basic Definitions

2.3 Axiomatic Definition of Boolean Algebra

2.4 Basic Theorems and Properties of Boolean Algebra

2.5 Boolean Functions

2.6 Canonical and Standard Forms

# **Table of Contents**

2.7 Other Logic Operations

2.8 Digital Logic Gates

2.9 Integrated Circuits

## **3 GateLevel Minimization**

3.1 Introduction

3.2 The Map Method

3.3 FourVariable KMap

3.4 ProductofSums Simplification

3.5 Don'tCare Conditions

3.6 NAND and NOR Implementation

3.7 Other TwoLevel Implementations

3.8 ExclusiveOR Function

3.9 Hardware Description Languages (HDLs)

3.10 Truth Tables in HDLs

## **4 Combinational Logic**

4.1 Introduction

4.2 Combinational Circuits

4.3 Analysis of Combinational Circuits

4.4 Design Procedure

4.5 Binary AdderSubtractor

4.6 Decimal Adder

4.7 Binary Multiplier

4.8 Magnitude Comparator

4.9 Decoders

4.10 Encoders

4.11 Multiplexers

4.12 HDL Models of Combinational Circuits

# **Table of Contents**

- 4.13 Behavioral Modeling
- 4.14 Writing a Simple Testbench
- 4.15 Logic Simulation

## **5 Synchronous Sequential Logic**

- 5.1 Introduction
- 5.2 Sequential Circuits
- 5.3 Storage Elements: Latches
- 5.4 Storage Elements: FlipFlops
- 5.5 Analysis of Clocked Sequential Circuits
- 5.6 Synthesizable HDL Models of Sequential Circuits
- 5.7 State Reduction and Assignment
- 5.8 Design Procedure

## **6 Registers and Counters**

- 6.1 Registers
- 6.2 Shift Registers
- 6.3 Ripple Counters
- 6.4 Synchronous Counters
- 6.5 Other Counters
- 6.6 HDL Models of Registers and Counters

## **7 Memory and Programmable Logic**

- 7.1 Introduction
- 7.2 RandomAccess Memory
- 7.3 Memory Decoding
- 7.4 Error Detection and Correction
- 7.5 ReadOnly Memory
- 7.6 Programmable Logic Array
- 7.7 Programmable Array Logic

# **Table of Contents**

7.8 Sequential Programmable Devices

## **8 Design at the Register Transfer Level**

8.1 Introduction

8.2 Register Transfer Level (RTL) Notation

8.3 RTL Descriptions

8.4 Algorithmic State Machines (ASMs)

8.5 Design Example (ASMD CHART)

8.6 HDL Description of Design Example

8.7 Sequential Binary Multiplier

8.8 Control Logic

8.9 HDL Description of Binary Multiplier

8.10 Design with Multiplexers

8.11 RaceFree Design (Software Race Conditions)

8.12 LatchFree Design (Why Waste Silicon?)

8.13 SystemVerilogAn Introduction

## **9 Laboratory Experiments with Standard ICs and FPGAs**

9.1 Introduction to Experiments

9.2 Experiment 1: Binary and Decimal Numbers

9.3 Experiment 2: Digital Logic Gates

9.4 Experiment 3: Simplification of Boolean Functions

9.5 Experiment 4: Combinational Circuits

9.6 Experiment 5: Code Converters

9.7 Experiment 6: Design with Multiplexers

9.8 Experiment 7: Adders and Subtractors

9.9 Experiment 8: FlipFlops

9.10 Experiment 9: Sequential Circuits

9.11 Experiment 10: Counters

# **Table of Contents**

- 9.12 Experiment 11: Shift Registers
- 9.13 Experiment 12: Serial Addition
- 9.14 Experiment 13: Memory Unit
- 9.15 Experiment 14: Lamp Handball
- 9.16 Experiment 15: ClockPulse Generator
- 9.17 Experiment 16: Parallel Adder and Accumulator
- 9.18 Experiment 17: Binary Multiplier
- 9.19 HDL Simulation Experiments and Rapid Prototyping with  
FPGAs

## **10 Standard Graphic Symbols**

- 10.1 RectangularShape Symbols
- 10.2 Qualifying Symbols
- 10.3 Dependency Notation
- 10.4 Symbols for Combinational Elements
- 10.5 Symbols for FlipFlops
- 10.6 Symbols for Registers
- 10.7 Symbols for Counters
- 10.8 Symbol for RAM

**Appendix**

**Answers to Selected Problems**

**Index**

**Back Cover**