

GLOBAL
EDITION



Principles of Electric Circuits

Conventional Current

TENTH EDITION

Thomas L. Floyd • David M. Buchla



PRINCIPLES OF ELECTRIC CIRCUITS

Conventional Current

**Tenth Edition
Global Edition**

**Thomas L. Floyd
David M. Buchla**



Principles of Electric Circuits: Conventional Current, Global Edition

Table of Contents

Cover

Title Page

Copyright

Dedication

Preface

Contents

1. Quantities and Units

11 Units of Measurement

12 Scientific Notation

13 Engineering Notation and Metric Prefixes

14 Metric Unit Conversions

15 Measured Numbers

2. Voltage, Current, and Resistance

21 Atomic Structure

22 Electrical Charge

23 Voltage

24 Current

25 Resistance

26 The Electric Circuit

27 Basic Circuit Measurements

28 Electrical Safety

Application Activity

3. Ohms Law

31 The Relationship of Current, Voltage, and Resistance

32 Current Calculations

33 Voltage Calculations

34 Resistance Calculations

Table of Contents

35 Introduction to Troubleshooting

Application Activity

4. Energy and Power

41 Energy and Power

42 Power in an Electric Circuit

43 Resistor Power Ratings

44 Energy Conversion and Voltage Drop in Resistance

45 Power Supplies and Batteries

Application Activity

5. Series Circuits

51 Resistors in Series

52 Total Series Resistance

53 Current in a Series Circuit

54 Application of Ohms Law

55 Voltage Sources in Series

56 Kirchhoffs Voltage Law

57 Voltage Dividers

58 Power in Series Circuits

59 Voltage Measurements

510 Troubleshooting

Application Activity

6. Parallel Circuits

61 Resistors in Parallel

62 Voltage in a Parallel Circuit

63 Kirchhoffs Current Law

64 Total Parallel Resistance

65 Application of Ohms Law

66 Current Sources in Parallel

67 Current Dividers

68 Power in Parallel Circuits

69 Parallel Circuit Applications

610 Troubleshooting

Application Activity

Table of Contents

7. Series-Parallel Circuits

- 71 Identifying Series-Parallel Relationships
- 72 Analysis of Series-Parallel Resistive Circuits
- 73 Voltage Dividers with Resistive Loads
- 74 Loading Effect of a Voltmeter
- 75 Ladder Networks
- 76 The Wheatstone Bridge
- 77 Troubleshooting
- Application Activity

8. Circuit Theorems and Conversions

- 81 The DC Voltage Source
- 82 The Current Source
- 83 Source Conversions
- 84 The Superposition Theorem
- 85 Thevenins Theorem
- 86 Nortons Theorem
- 87 Maximum Power Transfer Theorem
- 8–8 Delta-to-Wye (-to-Y) and Wye-to-Delta (Y-to-) Conversions
- Application Activity

9. Branch, Loop, and Node Analyses

- 91 Simultaneous Equations in Circuit Analysis
- 92 Branch Current Method
- 93 Loop Current Method
- 94 Node Voltage Method
- Application Activity

10. Magnetism and Electromagnetism

- 101 The Magnetic Field
- 102 Electromagnetism
- 103 Electromagnetic Devices
- 104 Magnetic Hysteresis
- 105 Electromagnetic Induction
- 106 The DC Generator
- 107 The DC Motor

Table of Contents

Application Activity

11. Introduction to Alternating Current and Voltage

111 The Sinusoidal Waveform

112 Sinusoidal Voltage and Current Values

113 Angular Measurement of a Sine Wave

114 The Sine Wave Formula

115 Introduction to Phasors

116 Analysis of AC Circuits

117 The Alternator (AC Generator)

118 The AC Motor

119 Nonsinusoidal Waveforms

1110 The Oscilloscope

Application Activity

12. Capacitors

121 The Basic Capacitor

122 Types of Capacitors

123 Series Capacitors

124 Parallel Capacitors

125 Capacitors in DC Circuits

126 Capacitors in AC Circuits

127 Capacitor Applications

128 Switched-Capacitor Circuits

Application Activity

13. RC Circuits

131 The Complex Number System

Part 1. Series Circuits

132 Sinusoidal Response of Series RC Circuits

133 Impedance of Series RC Circuits

134 Analysis of Series RC Circuits

Part 2. Parallel Circuits

135 Impedance and Admittance of Parallel RC Circuits

136 Analysis of Parallel RC Circuits

Part 3. Series-Parallel Circuits

Table of Contents

137 Analysis of Series-Parallel RC Circuits

Part 4. Special Topics

138 Power in RC Circuits

139 Basic Applications

1310 Troubleshooting

Application Activity

14. Inductors

141 The Basic Inductor

142 Types of Inductors

143 Series and Parallel Inductors

144 Inductors in DC Circuits

145 Inductors in AC Circuits

146 Inductor Applications

Application Activity

15. RL Circuits

Part 1. Series Circuits

151 Sinusoidal Response of Series RL Circuits

152 Impedance of Series RL Circuits

153 Analysis of Series RL Circuits

Part 2. Parallel Circuits

154 Impedance and Admittance of Parallel RL Circuits

155 Analysis of Parallel RL Circuits

Part 3. Series-Parallel Circuits

156 Analysis of Series-Parallel RL Circuits

Part 4. Special Topics

157 Power in RL Circuits

158 Basic Applications

159 Troubleshooting

Application Activity

16. Transformers

161 Mutual Inductance

162 The Basic Transformer

163 Step-Up and Step-Down Transformers

164 Loading the Secondary

Table of Contents

165	Reflected Load
166	Impedance Matching
167	Transformer Ratings and Characteristics
168	Tapped and Multiple-Winding Transformers
169	Troubleshooting
	Application Activity
17.	RLC Circuits and Resonance
	Part 1. Series Circuits
171	Impedance of Series RLC Circuits
172	Analysis of Series RLC Circuits
173	Series Resonance
	Part 2. Parallel Circuits
174	Impedance of Parallel RLC Circuits
175	Analysis of Parallel RLC Circuits
176	Parallel Resonance
	Part 3. Series-Parallel Circuits
177	Analysis of Series-Parallel RLC Circuits
	Part 4. Special Topics
178	Bandwidth of Resonant Circuits
179	Applications
	Application Activity
18.	Passive Filters
181	Low-Pass Filters
182	High-Pass Filters
183	Band-Pass Filters
184	Band-Stop Filters
	Application Activity
19.	Circuit Theorems in AC Analysis
191	The Superposition Theorem
192	Thevenins Theorem
193	Nortons Theorem
194	Maximum Power Transfer Theorem
	Application Activity
20.	Time Response of Reactive Circuits

Table of Contents

201	The RC Integrator
202	Response of an RC Integrator to a Single Pulse
203	Response of RC Integrators to Repetitive Pulses
204	Response of an RC Differentiator to a Single Pulse
205	Response of RC Differentiators to Repetitive Pulses
206	Response of RL Integrators to Pulse Inputs
207	Response of RL Differentiators to Pulse Inputs
208	Relationship of Time Response to Frequency Response
209	Troubleshooting
	Application Activity
21.	Three-Phase Systems in Power Applications
211	Generators in Power Applications
212	Types of Three-Phase Generators
213	Three-Phase Source/Load Analysis
214	Three-Phase Power
Appendices	
	Appendix A. Table of Standard Resistor Values
	Appendix B. Derivations
	Appendix C. Capacitor Label Coding
	Appendix D. NI Multisim for Circuit Simulation
Answers to Odd-Numbered Problems	
Glossary	
Index	