




TWELFTH EDITION



HUGHES

ELECTRICAL & ELECTRONIC TECHNOLOGY

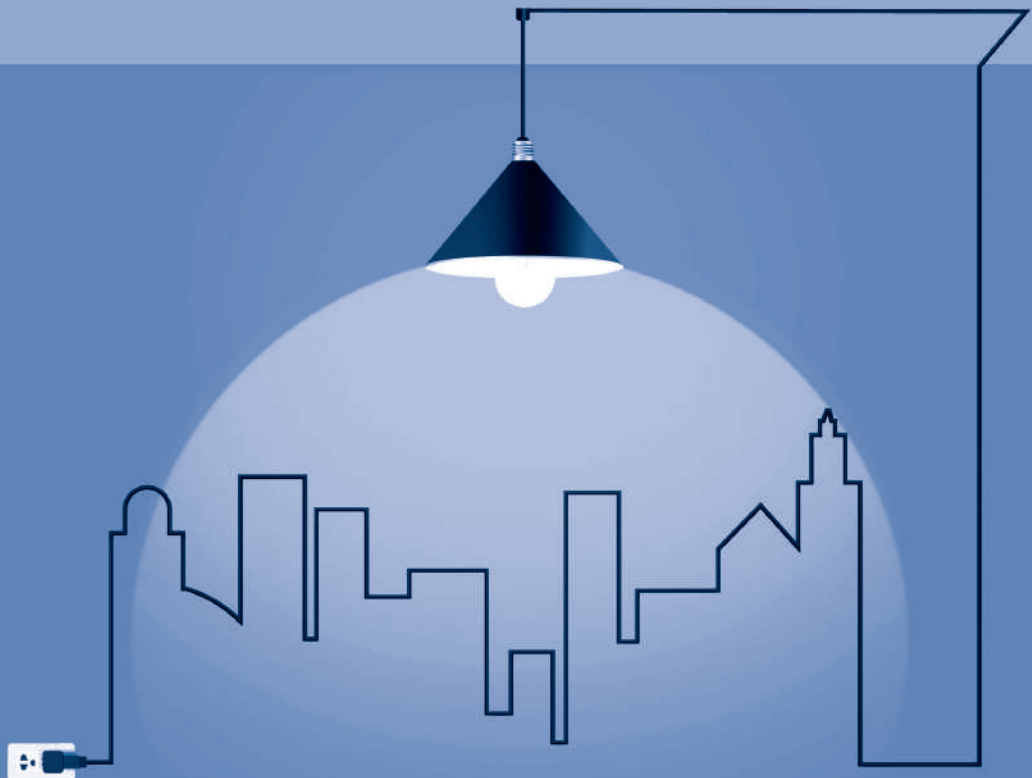REVISED BY JOHN HILEY, KEITH BROWN & IAN MCKENZIE SMITH



HUGHES
ELECTRICAL
& ELECTRONIC
TECHNOLOGY

Electrical and Electronic Technology

Table of Contents

Cover

Title Page

Copyright Page

Short Contents

Contents

Prefaces

Section 1 Electrical Principles

1 International System of Measurement

1.1 The International System

1.2 SI derived units

1.3 Unit of turning moment or torque

1.4 Unit of work or energy

1.5 Unit of power

1.6 Efficiency

1.7 Temperature

Summary of important formulae

Terms and concepts

2 Introduction to Electrical Systems

2.1 Electricity and the engineer

2.2 An electrical system

2.3 Electric charge

2.4 Movement of electrons

2.5 Current flow in a circuit

2.6 Electromotive force and potential difference

2.7 Electrical units

2.8 Ohms law

2.9 Resistors

2.10 Resistor coding

2.11 Conductors and insulators

Table of Contents

2.12 The electric circuit in practice

Summary of important formulae

Terms and concepts

3 Simple DC Circuits

3.1 Series circuits

3.2 Parallel networks

3.3 Series circuits versus parallel networks

3.4 Kirchhoffs laws

3.5 Power and energy

3.6 Resistivity

3.7 Temperature coefficient of resistance

3.8 Temperature rise

Summary of important formulae

Terms and concepts

4 Network Theorems

4.1 New circuit analysis techniques

4.2 Kirchhoffs laws and network solution

4.3 Mesh analysis

4.4 Nodal analysis

4.5 Superposition theorem

4.6 Thévenins theorem

4.7 The constant-current generator

4.8 Nortons theorem

4.9 Deltastar transformation

4.10 Stardelta transformation

4.11 II and T networks

4.12 Maximum power transfer

Summary of important formulae

Terms and concepts

5 Capacitance and Capacitors

5.1 Capacitors

5.2 Hydraulic analogy

5.3 Charge and voltage

5.4 Capacitance

Table of Contents

- 5.5 Capacitors in parallel
- 5.6 Capacitors in series
- 5.7 Distribution of voltage across capacitors in series
- 5.8 Capacitance and the capacitor
- 5.9 Electric fields
- 5.10 Electric field strength and electric flux density
- 5.11 Relative permittivity
- 5.12 Capacitance of a multi-plate capacitor
- 5.13 Composite-dielectric capacitors
- 5.14 Charging and discharging currents
- 5.15 Growth and decay
- 5.16 Analysis of growth and decay
- 5.17 Discharge of a capacitor through a resistor
- 5.18 Transients in CR networks
- 5.19 Energy stored in a charged capacitor
- 5.20 Force of attraction between oppositely charged plates
- 5.21 Dielectric strength
- 5.22 Leakage and conduction currents in capacitors
- 5.23 Displacement current in a dielectric
- 5.24 Types of capacitor and capacitance
- Summary of important formulae
- Terms and concepts

6 Electromagnetism

- 6.1 Magnetic field
- 6.2 Direction of magnetic field
- 6.3 Characteristics of lines of magnetic flux
- 6.4 Magnetic field due to an electric current
- 6.5 Magnetic field of a solenoid
- 6.6 Force on a current-carrying conductor
- 6.7 Force determination
- 6.8 Electromagnetic induction
- 6.9 Direction of induced e.m.f.
- 6.10 Magnitude of the generated or induced e.m.f.
- 6.11 Magnitude of e.m.f. induced in a coil
- Summary of important formulae

Table of Contents

Terms and concepts

7 Simple Magnetic Circuits

- 7.1 Introduction to magnetic circuits
- 7.2 Magnetomotive force and magnetic field strength
- 7.3 Permeability of free space or magnetic constant
- 7.4 Relative permeability
- 7.5 Reluctance
- 7.6 Ohms law for a magnetic circuit
- 7.7 Determination of the B/H characteristic
- 7.8 Comparison of electromagnetic and electrostatic terms
- Summary of important formulae

Terms and concepts

8 Inductance in a DC Circuit

- 8.1 Inductive and non-inductive circuits
- 8.2 Unit of inductance
- 8.3 Inductance in terms of flux-linkages per ampere
- 8.4 Factors determining the inductance of a coil
- 8.5 Ferromagnetic-cored inductor in a d.c. circuit
- 8.6 Growth in an inductive circuit
- 8.7 Analysis of growth
- 8.8 Analysis of decay
- 8.9 Transients in LR networks
- 8.10 Energy stored in an inductor
- 8.11 Mutual inductance
- 8.12 Coupling coefficient
- 8.13 Coils connected in series
- 8.14 Types of inductor and inductance
- Summary of important formulae

Terms and concepts

9 Alternating Voltage and Current

- 9.1 Alternating systems
- 9.2 Generation of an alternating e.m.f.
- 9.3 Waveform terms and definitions
- 9.4 Relationship between frequency, speed and number of pole pairs

Table of Contents

- 9.5 Average and r.m.s. values of an alternating current
- 9.6 Average and r.m.s. values of sinusoidal currents and voltages
- 9.7 Average and r.m.s. values of non-sinusoidal currents and voltages
- 9.8 Representation of an alternating quantity by a phasor
- 9.9 Addition and subtraction of sinusoidal alternating quantities
- 9.10 Phasor diagrams drawn with r.m.s. values instead of maximum values
- 9.11 Alternating system frequencies in practice
- Summary of important formulae
- Terms and concepts

10 Single-phase Series Circuits

- 10.1 Basic a.c. circuits
- 10.2 Alternating current in a resistive circuit
- 10.3 Alternating current in an inductive circuit
- 10.4 Current and voltage in an inductive circuit
- 10.5 Mechanical analogy of an inductive circuit
- 10.6 Resistance and inductance in series
- 10.7 Alternating current in a capacitive circuit
- 10.8 Current and voltage in a capacitive circuit
- 10.9 Analogies of a capacitance in an a.c. circuit
- 10.10 Resistance and capacitance in series
- 10.11 Alternating current in an RLC circuit
- Summary of important formulae
- Terms and concepts

11 Single-phase Parallel Networks

- 11.1 Basic a.c. parallel circuits
- 11.2 Simple parallel circuits
- 11.3 Parallel impedance circuits
- 11.4 Polar impedances
- 11.5 Polar admittances
- Summary of important formulae
- Terms and concepts

12 Complex Notation

- 12.1 The j operator
- 12.2 Addition and subtraction of phasors

Table of Contents

- 12.3 Voltage, current and impedance
- 12.4 Admittance, conductance and susceptance
- 12.5 RL series circuit admittance
- 12.6 RC series circuit admittance
- 12.7 Parallel admittance
- 12.8 Calculation of power using complex notation
- 12.9 Power and voltamperes
- 12.10 Complex power
- Summary of important formulae
- Terms and concepts

13 Power in AC Circuits

- 13.1 The impossible power
- 13.2 Power in a resistive circuit
- 13.3 Power in a purely inductive circuit
- 13.4 Power in a purely capacitive circuit
- 13.5 Power in a circuit with resistance and reactance
- 13.6 Power factor
- 13.7 Active and reactive currents
- 13.8 The practical importance of power factor
- 13.9 Power factor improvement or correction
- 13.10 Parallel loads
- 13.11 Measurement of power in a single-phase circuit
- Summary of important formulae
- Terms and concepts

14 Resonance in AC Circuits

- 14.1 Introduction
- 14.2 Frequency variation in a series RLC circuit
- 14.3 The resonant frequency of a series RLC circuit
- 14.4 The current in a series RLC circuit
- 14.5 Voltages in a series RLC circuit
- 14.6 Quality factor Q
- 14.7 Oscillation of energy at resonance
- 14.8 Mechanical analogy of a resonant circuit
- 14.9 Series resonance using complex notation
- 14.10 Bandwidth

Table of Contents

- 14.11 Selectivity
- 14.12 Parallel resonance
- 14.13 Current magnification
- 14.14 Parallel and series equivalents
- 14.15 The two-branch parallel resonant circuit
- Summary of important formulae
- Terms and concepts

15 Network Theorems Applied to AC Networks

- 15.1 One stage further
- 15.2 Kirchhoffs laws and network solution
- 15.3 Nodal analysis (Node Voltage method)
- 15.4 Superposition theorem
- 15.5 Thévenins theorem
- 15.6 Nortons theorem
- 15.7 Stardelta transformation
- 15.8 Deltastar transformation
- 15.9 Maximum power transfer
- Terms and concepts

Section 2 Electronic Engineering

16 Electronic Systems

- 16.1 Introduction to systems
- 16.2 Electronic systems
- 16.3 Basic amplifiers
- 16.4 Basic attenuators
- 16.5 Block diagrams
- 16.6 Layout of block diagrams
- Summary of important formulae
- Terms and concepts

17 Passive Filters

- 17.1 Introduction
- 17.2 Types of filter
- 17.3 Frequency response
- 17.4 Logarithms
- 17.5 Log scales

Table of Contents

- 17.6 The decibel (dB)
- 17.7 The low-pass or lag circuit
- 17.8 The high-pass or lead circuit
- 17.9 Passband (or bandpass) filter
- 17.10 Stopband (or bandstop) filters
- 17.11 Bode plots
- 17.12 2-port Networks
- Summary of important formulae
- Terms and concepts

18 Amplifier Equivalent Networks

- 18.1 Amplifier constant-voltage equivalent networks
- 18.2 Amplifier constant-current equivalent networks
- 18.3 Logarithmic units
- 18.4 Frequency response
- 18.5 Feedback
- 18.6 Effect of feedback on input and output resistances
- 18.7 Effect of feedback on bandwidth
- 18.8 Distortion
- Summary of important formulae
- Terms and concepts

19 Semiconductor Materials

- 19.1 Introduction
- 19.2 Atomic structure
- 19.3 Covalent bonds
- 19.4 An n-type semiconductor
- 19.5 A p-type semiconductor
- 19.6 Junction diode
- 19.7 Construction and static characteristics of a junction diode
- Terms and concepts

20 Rectifiers and Amplifier Circuits

- 20.1 Rectifier circuits
- 20.2 Half-wave rectifier
- 20.3 Full-wave rectifier network
- 20.4 Bridge rectifier network

Table of Contents

20.5 Smoothing
20.6 Zener diode
20.7 Bipolar junction transistor
20.8 Construction of bipolar transistor
20.9 Common-base and common-emitter circuits
20.10 Static characteristics for a common-base circuit
20.11 Static characteristics for a common-emitter circuit
20.12 Relationship between α and β
20.13 Load line for a transistor
20.14 Transistor as an amplifier
20.15 Circuit component selection
20.16 Equivalent circuits of a transistor
20.17 Hybrid parameters
20.18 Limitations to the bipolar junction transistor
20.19 Stabilizing voltages supplies
20.20 Transistor as a switch
20.21 Field effect transistor (FET)
20.22 JUGFET
20.23 IGFET
20.24 Static characteristics of a FET
20.25 Equivalent circuit of a FET
20.26 The FET as a switch
20.27 Cascaded amplifiers
20.28 Integrated circuits
20.29 Operational amplifiers
20.30 The inverting operational amplifier
20.31 The summing amplifier
20.32 The non-inverting amplifier
20.33 Differential amplifiers
20.34 Common-mode rejection ratio
Summary of important formulae
Terms and concepts

21 Interfacing Digital and Analogue Systems

21.1 The need for conversion
21.2 Digital-to-analogue conversion

Table of Contents

- 21.3 D/A converter hardware
- 21.4 D/A converters in practice
- 21.5 R/2R ladder D/A converter
- 21.6 Analogue-to-digital conversion
- 21.7 Simple comparator
- 21.8 A/D converters
- 21.9 Converters in action
- Terms and concepts

22 Digital Numbers

- 22.1 Introduction
- 22.2 Binary numbers
- 22.3 Decimal to binary conversion
- 22.4 Binary addition
- 22.5 Binary subtraction
- 22.6 Binary multiplication
- 22.7 Binary division
- 22.8 Negative binary numbers
- 22.9 Signed binary addition
- 22.10 Signed binary subtraction
- 22.11 Signed binary multiplication
- 22.12 Signed binary division
- 22.13 The octal system
- 22.14 Hexadecimal numbers
- Terms and concepts

23 Digital Systems

- 23.1 Introduction to logic
- 23.2 Basic logic statements or functions
- 23.3 The OR function
- 23.4 The AND function
- 23.5 The EXCLUSIVE-OR function
- 23.6 The NOT function
- 23.7 Logic gates
- 23.8 The NOR function
- 23.9 The NAND function
- 23.10 Logic networks

Table of Contents

- 23.11 Combinational logic
- 23.12 Gate standardization
- 23.13 Karnaugh maps for simplifying combinational logic
- 23.14 Timing diagrams
- 23.15 Combinational and sequential logic circuits
- 23.16 Synchronous and asynchronous sequential circuits
- 23.17 Basic storage elements
- 23.18 Integrated circuit logic gates
- 23.19 Programmable logic and hardware description languages
- Summary of important formulae
- Terms and concepts

24 Signals

- 24.1 Classification of signals
- 24.2 Representation of a signal by a continuum of impulses
- 24.3 Impulse response
- 24.4 Convolution sum for discrete-time systems
- 24.5 Convolution integral for continuous-time systems
- 24.6 Deconvolution
- 24.7 Relation between impulse response and unit step response
- 24.8 Step and impulse responses of discrete-time systems
- Summary of important formulae
- Terms and concepts

25 Data Transmission and Signals

- 25.1 Transmission of information
- 25.2 Analogue signals
- 25.3 Digital signals
- 25.4 Bandwidth
- 25.5 Modulation
- 25.6 Filters
- 25.7 Demodulation
- 25.8 Amplifying signals
- 25.9 Digital or analogue?
- Terms and concepts

26 Communications

Table of Contents

- 26.1 Basic concepts
- 26.2 Information theory for source coding
- 26.3 Data communication systems
- 26.4 Coding for efficient transmission
- 26.5 Source coding
- Summary of important formulae
- Terms and concepts

27 Fibreoptics

- 27.1 Introduction
- 27.2 Fibre loss
- 27.3 Refraction
- 27.4 Light acceptance
- 27.5 Attenuation
- 27.6 Bandwidth
- 27.7 Modulation
- 27.8 Optical fibre systems
- Summary of important formulae
- Terms and concepts

Section 3 Power Engineering

28 Multiphase Systems

- 28.1 Disadvantages of the single-phase system
- 28.2 Generation of three-phase e.m.f.s
- 28.3 Delta connection of three-phase windings
- 28.4 Star connection of three-phase windings
- 28.5 Voltages and currents in a star-connected system
- 28.6 Voltages and currents in a delta-connected system
- 28.7 Power in a three-phase system with a balanced load
- 28.8 Measurement of active power in a three-phase, three-wire system
- 28.9 Power factor measurement by means of two wattmeters
- 28.10 Two-phase systems
- Summary of important formulae
- Terms and concepts

29 Transformers

- 29.1 Introduction

Table of Contents

- 29.2 Core factors
- 29.3 Principle of action of a transformer
- 29.4 EMF equation of a transformer
- 29.5 Phasor diagram for a transformer on no load
- 29.6 Phasor diagram for an ideal loaded transformer
- 29.7 Useful and leakage fluxes in a transformer
- 29.8 Leakage flux responsible for the inductive reactance of a transformer
- 29.9 Methods of reducing leakage flux
- 29.10 Equivalent circuit of a transformer
- 29.11 Phasor diagram for a transformer on load
- 29.12 Approximate equivalent circuit of a transformer
- 29.13 Simplification of the approximate equivalent circuit of a transformer
- 29.14 Voltage regulation of a transformer
- 29.15 Efficiency of a transformer
- 29.16 Condition for maximum efficiency of a transformer
- 29.17 Open-circuit and short-circuit tests on a transformer
- 29.18 Calculation of efficiency from the open-circuit and short-circuit tests
- 29.19 Calculation of the voltage regulation from the short-circuit test
- 29.20 Three-phase core-type transformers
- 29.21 Auto-transformers
- 29.22 Current transformers
- 29.23 Waveform of the magnetizing current of a transformer
- 29.24 Air-cored transformer
- Summary of important formulae
- Terms and concepts

30 Introduction to Machine Theory

- 30.1 The role of the electrical machine
- 30.2 Conversion process in a machine
- 30.3 Methods of analysis of machine performance
- 30.4 Magnetic field energy
- 30.5 Simple analysis of force of alignment
- 30.6 Energy balance
- 30.7 Division of converted energy and power
- 30.8 Force of alignment between parallel magnetized surfaces
- 30.9 Rotary motion

Table of Contents

30.10 Reluctance motor

30.11 Doubly excited rotating machines

Summary of important formulae

Terms and concepts

31 AC Synchronous Machine Windings

31.1 General arrangement of synchronous machines

31.2 Types of rotor construction

31.3 Stator windings

31.4 Expression for the e.m.f. of a stator winding

31.5 Production of rotating magnetic flux by three-phase currents

31.6 Analysis of the resultant flux due to three-phase currents

31.7 Reversal of direction of rotation of the magnetic flux

Summary of important formulae

Terms and concepts

32 Characteristics of AC Synchronous Machines

32.1 Armature reaction in a three-phase synchronous generator

32.2 Voltage regulation of a synchronous generator

32.3 Synchronous impedance

32.4 Parallel operation of synchronous generators

32.5 Three-phase synchronous motor: principle of action

32.6 Advantages and disadvantages of the synchronous motor

Terms and concepts

33 Induction Motors

33.1 Principle of action

33.2 Frequency of rotor e.m.f. and current

33.3 The equivalent circuit of the three-phase induction motor

33.4 Mechanical power and torque

33.5 The torque/speed curve and effect of rotor resistance

33.6 Experimental tests to obtain motor equivalent circuit parameters

33.7 Starting torque

33.8 Starting of a three-phase induction motor fitted with a cage rotor

33.9 Comparison of cage and slip-ring rotors

33.10 Braking

33.11 Single-phase induction motors

Table of Contents

- 33.12 Capacitor-run induction motors
- 33.13 Split-phase motors
- 33.14 Shaded-pole motors
- 33.15 Variable speed operation of induction motors
- Summary of important formulae
- Terms and concepts

34 Electrical Energy Systems

- 34.1 Energy units
- 34.2 Forms of energy
- 34.3 Energy conversion and quality of energy
- 34.4 Demand for electricity and the National Grid
- 34.5 Generating plant
- 34.6 Nuclear power
- 34.7 Renewable energy
- 34.8 Distributed/Embedded generation
- 34.9 Demand management
- 34.10 The cost of generating electricity
- Summary of important formulae
- Terms and concepts

35 Power Systems

- 35.1 System representation
- 35.2 Power system analysis
- 35.3 Voltage-drop calculations
- 35.4 The medium-length line
- 35.5 The per-unit method
- 35.6 Per-unit impedance
- 35.7 Base power SB or MV AB
- 35.8 Faults in a power system
- 35.9 Representation of a grid connection
- 35.10 Transmission Line effects
- Summary of important formulae
- Terms and concepts

36 Direct-current Machines

- 36.1 General arrangement of a d.c. machine

Table of Contents

- 36.2 Double-layer drum windings
- 36.3 Calculation of e.m.f. generated in an armature winding
- 36.4 Armature reaction
- 36.5 Armature reaction in a d.c. motor
- 36.6 Commutation
- Summary of important formulae
- Terms and concepts

37 Direct-current Motors

- 37.1 Armature and field connections
- 37.2 A d.c. machine as generator or motor
- 37.3 Speed of a motor
- 37.4 Torque of an electric motor
- 37.5 Speed characteristics of electric motors
- 37.6 Torque characteristics of electric motors
- 37.7 Speed control of d.c. motors
- Summary of important formulae
- Terms and concepts

38 Control System Motors

- 38.1 Review
- 38.2 Motors for regulators
- 38.3 RPC system requirements
- 38.4 Geneva cam
- 38.5 The stepping (or stepper) motor
- 38.6 The variable-reluctance motor
- 38.7 The hybrid stepping motor
- 38.8 Drive circuits
- Terms and concepts

39 Motor Selection and Efficiency

- 39.1 Selecting a motor
- 39.2 Speed
- 39.3 Power rating and duty cycles
- 39.4 Load torques
- 39.5 The motor and its environment
- 39.6 Machine efficiency

Table of Contents

- 39.7 Hysteresis
- 39.8 Current-ring theory of magnetism
- 39.9 Hysteresis loss
- 39.10 Losses in motors and generators
- 39.11 Efficiency of a d.c. motor
- 39.12 Approximate condition for maximum efficiency
- 39.13 Determination of efficiency
- Terms and concepts

40 Power Electronics

- 40.1 Introductory
- 40.2 Thyristor
- 40.3 Some thyristor circuits
- 40.4 Limitations to thyristor operation
- 40.5 The thyristor in practice
- 40.6 The fully controlled a.c./d.c. converter
- 40.7 AC/DC inversion
- 40.8 Switching devices in inverters
- 40.9 Three-phase rectifier networks
- 40.10 The three-phase fully controlled converter
- 40.11 Inverter-fed induction motors
- 40.12 Soft-starting induction motors
- 40.13 DC to DC conversion switched-mode power supplies
- Summary of important formulae
- Terms and concepts

Section 4 Measurements, Sensing and Actuation

41 Control Systems, Sensors and Actuators

- 41.1 Introduction
- 41.2 Open-loop and closed-loop systems
- 41.3 Damping
- 41.4 Components of a control system
- 41.5 Transfer function
- 41.6 Regulators and servomechanisms
- 41.7 Types of control
- 41.8 Sensors

Table of Contents

41.9 Actuators

Terms and concepts

42 Electronic Measuring Instruments and Devices

42.1 Introduction to analogue and electronic instruments

42.2 Digital electronic voltmeters

42.3 Digital electronic ammeters and wattmeters

42.4 Graphical display devices

42.5 The vacuum diode

42.6 The vacuum triode

42.7 Modern applications of vacuum-tube technology

42.8 Cathode-ray tube

42.9 Deflecting systems of a cathode-ray tube

42.10 Cathode-ray oscilloscope

42.11 Digital oscilloscope

42.12 Use of the oscilloscope in waveform measurement

42.13 Oscilloscope connection

Terms and concepts

Appendix: Symbols, Abbreviations, Denitions and Diagrammatic

Symbols

Answers to Exercises

Index